



YBN University, Ranchi

Problems on Rectifiers

Important mathematical expressions on rectifiers:

1. Half wave rectifier

$$v_i(t) = V_m \sin \omega t$$

$$i_i(t) = I_m \sin \omega t$$

Where, V_m and I_m are instantaneous values or peak values of input voltage and current respectively, ω is the input signal frequency in rad/sec. $\omega = 2\pi f$, f is the frequency of the input signal in Hz.

Case(i): If diode and transformer are ideal. i.e., $R_f = R_s = 0$.

Given V_m , find I_m

$$I_{DC} = \frac{I_m}{\pi}$$

$$V_{DC} = \frac{V_m}{\pi} \text{ or } I_{DC} \times R_L$$

$$I_{rms} = \frac{I_m}{2}$$

$$V_{rms} = \frac{V_m}{2} \text{ or } I_{rms} \times R_L$$

$$\text{Ripple factor}(\gamma) = \frac{\sqrt{V_{rms}^2 - V_{DC}^2}}{V_{DC}} = 1.21 \text{ (Ideally)}$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{AC}} \times 100 = 40.6\% \text{ (Ideally)}$$

$$PIV = V_m$$

Case(ii): Non-Zero R_f and $R_s = 0$.

Given V_m , find I_m

$$I_m = \frac{V_m}{R_f + R_L}$$

$$I_{DC} = \frac{I_m}{\pi}$$

$$V_{DC} = I_{DC} \times (R_L + r_f)$$

$$I_{rms} = \frac{I_m}{2}$$

$$V_{rms} = I_{rms} \times (R_L + R_f)$$

$$\text{Ripple factor}(\gamma) = \frac{\sqrt{I_{rms}^2 - I_{DC}^2}}{I_{DC}} \times R_L$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{I_{DC}^2 \times R_L}{I_{rms}^2 \times (R_f + R_L)} \times 100$$

$$PIV = V_m$$

$V_{DC} = I_{DC}(R_s + R_L)$
Dr. Vinita Kumara, YBN University, Ranchi

$$I_{rms} = \frac{I_m}{2}$$

$$V_{rms} = I_{rms} \times (R_L + R_s)$$

Case(iii): non-zero R_s and

$R_f=0$. Given V_m , find I_m

$$I_m = \frac{V_m}{R_s + R_L}$$

$$I_{DC} = \frac{I_m}{\pi}$$

$$\text{Ripple factor}(\gamma) = \frac{\sqrt{I_{\text{rms}}^2 - I_{\text{DC}}^2}}{I_{\text{DC}}} = \frac{I_{\text{rms}}^2 - I_{\text{DC}}^2}{P_{\text{DC}} I_{\text{DC}} I^2 \times R_L}$$

$$\text{Efficiency}(\eta) = \frac{P_{\text{DC}}}{P_{\text{AC}}} \times 100 = \frac{I_{\text{DC}}^2}{I_{\text{rms}}^2 (R_f + R_s + R_L)} \times 100$$

$$\text{PIV} = V_m$$

Case(iv): non-zero R_f and R_s .

Given V_m , find I_m

$$I_m = \frac{V_m}{R_f + R_s + R_L}$$

$$I_{\text{DC}} = \frac{I_m}{\pi}$$

$$V_{\text{DC}} = I_{\text{DC}} \times (R_f + R_s + R_L)$$

$$I_{\text{rms}} = \frac{I_m}{2}$$

$$V_{\text{rms}} = I_{\text{rms}} \times (R_f + R_s + R_L) = \frac{I_m}{2} \times (R_f + R_s + R_L)$$

$$\text{Ripple factor}(\gamma) = \frac{\sqrt{I_{\text{rms}}^2 - I_{\text{DC}}^2}}{I_{\text{DC}}} = \frac{I_{\text{rms}}^2 - I_{\text{DC}}^2}{P_{\text{DC}} I_{\text{DC}} I^2 \times R_L}$$

$$\text{Efficiency}(\eta) = \frac{P_{\text{DC}}}{P_{\text{AC}}} \times 100 = \frac{I_{\text{DC}}^2}{I_{\text{rms}}^2 (R_f + R_s + R_L)} \times 100$$

$$\text{PIV} = V_m$$

Half wave rectifier with C filter

time constant $T_d = C \times R_L$ Discharging

$$\text{Ripple factor}(\gamma) = \frac{1}{2\sqrt{3}fR_L C} \Rightarrow \frac{V_r(p-p)}{V_{\text{DC}}}$$

$$V_r(p-p) = \frac{V_p}{fR_L C}$$

$$V_{\text{DC}} = \left(1 - \frac{1}{2fR_L C}\right) V_p$$

Where, V_p is the rectified unfiltered output voltage across the load.

2. Full wave rectifier (2 diodes, with center tap transformer)

$$i(t) = V_m \sin \omega t$$

$$= I_m \sin \omega t$$

Where, V_m and I_m are instantaneous values or peak values of input voltage and current respectively, ω is the input signal frequency in rad/sec. $\omega = 2\pi f$, f is the frequency of the input signal in Hz.

Case(i): If diode and transformer is ideal. i.e., $R_f=R_s=0$.

Given V_m , find I_m

$$I_m = \frac{V_m}{R_L}$$

$$I_{DC} = \frac{2I_m}{\pi}$$

$$\frac{V_{DC}}{\sqrt{2}V_m} \times R_L = I_{rms}$$

or I

$$= \frac{I_m}{\sqrt{2}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \text{ or } I_{rms} \times R_L$$

$$\text{Ripple factor}(\gamma) = \frac{\sqrt{V_{\text{rms}}^2 - V_{\text{DC}}^2}}{V_{\text{DC}}} = 0.48(\text{Ideally})$$

$$\text{Efficiency}(\eta) = \frac{P_{\text{DC}}}{P_{\text{AC}}} \times 100 = 81.2\%(\text{Ideally})$$

$$\text{PIV} = 2V_m$$

Case(ii): Non-Zero R_f and

$R_s=0$. Given V_m , find I_m

$$I_m = \frac{V_m}{R_f + R_L}$$

$$I_{\text{DC}} = \frac{2I_m}{\pi}$$

$$V_{\text{DC}} = I_{\text{DC}} \times (R_L + r_f)$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

$$V_{\text{rms}} = I_{\text{rms}} \times (R_L + R_f)$$

$$\text{Ripple factor}(\gamma) = \frac{\sqrt{I_{\text{rms}}^2 - I_{\text{DC}}^2}}{I_{\text{DC}}} = \frac{I_m}{I_{\text{DC}}} \times \frac{\sqrt{I^2 - I_{\text{DC}}^2}}{I_{\text{DC}}}$$

$$\text{Efficiency}(\eta) = \frac{P_{\text{DC}}}{P_{\text{AC}}} \times 100 = \frac{I_{\text{DC}}^2 \times R_L}{I_{\text{rms}}^2 \times (R_f + R_L)} \times 100$$

$$\text{PIV} = 2V_m$$

Case(iii): non-zero R_s and $R_f=0$.

Given V_m , find I_m

$$I_m = \frac{V_m}{R_s + R_L}$$

$$I_{\text{DC}} = \frac{2I_m}{\pi}$$

$$V_{\text{DC}} = I_{\text{DC}} \times (R_L + R_s)$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

$$V_{\text{rms}} = I_{\text{rms}} \times (R_L + R_s)$$

$$\text{Ripple factor}(\gamma) = \frac{\sqrt{I_{\text{rms}}^2 - I_{\text{DC}}^2}}{I_{\text{DC}}} = \frac{I_m}{I_{\text{DC}}} \times \frac{\sqrt{I^2 - I_{\text{DC}}^2}}{I_{\text{DC}}}$$

$$\text{Efficiency}(\eta) = \frac{P_{\text{DC}}}{P_{\text{AC}}} \times 100 = \frac{I_{\text{DC}}^2 \times R_L}{I_{\text{rms}}^2 \times (R_s + R_L)} \times 100$$

$$\text{PIV} = 2V_m$$

Er. Vinita kumara, YBN University, Ranchi

$$\text{Ripple factor}(\gamma) = \frac{\sqrt{I^2 - I_{DC}^2}}{I_{DC}}$$

Case(iv): non-zero R_f and R_s . Given V_m , find I_m

$$I_m = \frac{V_m}{R_f + R_s + R_L}$$

$$I_{DC} = \frac{2I_m}{\pi}$$

$$V_{DC} = I_{DC} \times (R_f + R_s + R_L)$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$V_{rms} = I_{rms} \times (R_f + R_s + R_L)$$

$$\text{Efficiency } (\eta) = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{I_{DC}^2 \times R_L}{I_{rms}^2 (R_f + R_s + R_L)} \times 100$$

$$PIV = 2V_m$$

Full wave rectifier with C filter

$$\text{Ripple factor } (\gamma) = \frac{1}{V_p} \frac{d = \frac{V_{r(p-p)}}{V_{DC}} \text{ Discharging time constant } T = C \times R}{4\sqrt{3}fR_L C} \Rightarrow \frac{V_{r(p-p)}}{V_{DC}}$$

$$V_{r(p-p)} = \frac{V_p}{2fR_L C}$$

$$V_{DC} = \left(1 - \frac{1}{2fR_L C}\right) \left(\frac{V_p}{2}\right)$$

Where, V_p is the rectified unfiltered output voltage across the load.

3. Full wave rectifier (4 diodes, without center-tap transformer and bridge type connection of diodes)

$$v_i(t) = V_m \sin \omega t$$

$$i(t) = I_m \sin \omega t$$

Where, V_m and I_m are instantaneous values or peak values of input voltage and current respectively, ω is the input signal frequency in rad/sec.

$\omega = 2\pi f$, f is the frequency of the input signal in Hz.

Case(i): If diode and transformer is ideal. i.e., $R_f = R_s = 0$.

Given V_m , find I_m

$$I_{DC} = \frac{2I_m}{\pi}$$

$$V_{DC} = \frac{2V_m}{\pi} \text{ or } I_{DC} \times R_L$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \text{ or } I_{rms} \times R_L$$

$$\text{Ripple factor } (\gamma) = \frac{\sqrt{V_{rms}^2 - V_{DC}^2}}{V_{DC}} = 0.48 \text{ (Ideally)}$$

$$\text{Efficiency } (\eta) = \frac{P_{DC}}{P_{AC}} \times 100 = 81.2\% \text{ (Ideally)}$$

$$PIV = V_m$$

$$V_{\text{rms}} = I_{\text{rms}} \times (R_L + 2R_f)$$

Er. Vinita kumara, YBN University, Ranchi

$$\text{Ripple factor}(\gamma) = \frac{I_{\text{rms}}^2 - I_{\text{DC}}^2}{I_{\text{DC}}^2} \times R_L$$

$$\text{Efficiency}(\eta) = \frac{P_{\text{DC}}}{P_{\text{AC}}} \times 100 = \frac{I_{\text{DC}}^2 \times R_L}{I_{\text{rms}}^2 (2R_f + R_L)} \times 100$$

Case(ii): Non-Zero R_f and

$R_s=0$. Given V_m , find I_m

$$I_m = \frac{V_m}{2R_f + R_L}$$

$$I_{\text{DC}} = \frac{2I_m}{\pi}$$

$$V_{\text{DC}} = I_{\text{DC}} \times (R_L + 2R_f)$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

$$PIV = V_m$$

Case(iii): non-zero r_s and $r_f=0$.

Given v_m , find I_m

$$I_m = \frac{V_m}{R_s + R_L}$$

$$I_{DC} = \frac{2I_m}{\pi}$$

$$V_{DC} = I_{DC} \times (R_L + R_s)$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$V_{rms} = I_{rms} \times (R_L + R_s)$$

$$Ripple\ factor(\gamma) = \frac{\sqrt{I_{rms}^2 - I_{DC}^2}}{I_{DC}} = \frac{I_m}{I_{DC}} \times \frac{\sqrt{I_m^2 - I_{DC}^2}}{I_m}$$

$$Efficiency(\eta) = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{I_{DC}^2 \times R_L}{I_{rms}^2 \times (R_s + R_L)} \times 100$$

$$PIV = V_m$$

Case(iv): non-zero R_f and R_s .

Given v_m , find I_m

$$I_m = \frac{V_m}{2R_f + R_s + R_L}$$

$$I_{DC} = \frac{2I_m}{\pi}$$

$$V_{DC} = I_{DC} \times (2R_f + R_s + R_L)$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$V_{rms} = I_{rms} \times (2R_f + R_s + R_L)$$

$$Ripple\ factor(\gamma) = \frac{\sqrt{I_{rms}^2 - I_{DC}^2}}{I_{DC}} = \frac{I_m}{I_{DC}} \times \frac{\sqrt{I_m^2 - I_{DC}^2}}{I_m}$$

$$Efficiency(\eta) = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{I_{DC}^2 \times R_L}{I_{rms}^2 \times (2R_f + R_s + R_L)} \times 100$$

$$PIV = V_m$$

Full wave rectifier with C filter

Discharging time constant $T_d = C \times R_L$

$$Ripple\ factor(\gamma) = \frac{1}{4\sqrt{3}fR_L C} \Rightarrow \frac{V_r(p-p)}{V_{DC}}$$

$$V_r(p-p) = \frac{V_p}{2fR_L C}$$

$$V_{DC} = \left(1 - \frac{1}{2fR_L C}\right) \left(\frac{V_p}{2}\right)$$

Where, V_p is the rectified unfiltered output voltage across the load.

Note:

1. If primary voltage of the transformer is given with turns ratio, calculate the secondary voltage and then convert rms value into peak value (instantaneous value).

Example:

$v_p=230V$ with turns ratio

12:1($N_p:N_s$) w.k.t.

$$\frac{V_p}{V_s} = \frac{N_p}{N_s}$$

$$\text{Therefore, } V_s = \frac{N_s}{N_p} \times V_p \Rightarrow \left(\frac{1}{12}\right) \times 230 \Rightarrow 19.167 \text{ V}$$

V_s is the rms value of the secondary of the transformer.
Hence, convert into peak value.

$$V_m = \sqrt{2} \times V_s$$

2. If the rms value of the secondary voltage of the transformer is given, then convert into peak value.

Example:

If V_s is 200V-0V

$$V_s = 200\text{V and } v_m = \sqrt{2} \times V_s \Rightarrow 282.84\text{V}$$

3. For center tapped transformers Example 1:

$v_p = 230 \text{ V}$ with turns ratio 12:1:12

($N_p:N_s:N_p$) w.k.t.

$$\frac{V_p}{N_p} = \frac{V_s}{N_s}$$

Therefore, $V_s = \frac{N_s}{N_p} \times V_p \Rightarrow \left(\frac{1}{12}\right) \times 230 \Rightarrow 19.167 \text{ V}$

V_s is the rms value of the secondary of the transformer. Hence, convert into peak value.

$$v_m = \sqrt{2} \times \frac{V_s}{2}$$

NOTE: in the above expression, peak value is the $\sqrt{2}V_s$ divided by two, because the secondary voltage would be divided into two halves at upper part and lower part of the secondary of the center tap transformer.

Example 2:

If V_s is given as 200V-0V-200V

$$V_s = 200\text{V and } v_m = \sqrt{2} \times V_s \Rightarrow 282.84\text{V}$$

Example 3:

If V_s is given as 200V rms

NOTE: V_s is the total secondary voltage.

$$V_m = \sqrt{2} \times \frac{V_s}{2} \Rightarrow 141.2\text{V}$$

Example 4:

If V_s is given as 50V-0-50V peak value Then, $V_m = 50\text{V}$

Example 5:

If V_s is given as 100V peak value

Er. Vinita kumara, YBN University, Ranchi

$$\text{Then, } V_m = \frac{V_s}{\sqrt{2}} \Rightarrow 50V$$

Example 6:

If V_s is given as 100V peak to peak rms value

$$\text{Then, } V_m = \frac{\sqrt{2}V_s}{4} \Rightarrow 25V$$

Example 7:

If V_s is given as 100V peak to peak value

$$\text{Then, } V_m = \frac{V_s}{4} \Rightarrow 25V$$

4. If the peak to peak rms value of the secondary voltage of the transformer is given, then convert into peak value.

Example1:

If V_s is 300V peak to peak rms value

$$V_m = \frac{\sqrt{2}V_s}{2} \Rightarrow 212.13V$$

Example2:

If V_s is 300V peak to peak instantaneous value V_s is given

$$V_m = \frac{V_s}{2} \Rightarrow 150V$$

NOTE:

1. In half wave rectifier, there is only one pulse for every complete one cycle, hence, frequency of the output signal is same as the frequency of the input signal.
2. In full wave rectifier, there are two pulses for every complete one cycle, hence, the frequency of the output signal is two times that of the frequency of the input signal.

Solved Examples

P1. An ideal diode in an Half wave rectifier circuit energized by a 50V peak sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor.

Given data:

$$\text{HWR, } V_m = 50V, R_L$$

= 1KΩ **To find:**

$$I_{DC}, V_{DC}, I_{rms}, V_{rms}, \eta \text{ and } \gamma$$

Solution:

$$I_m = \frac{V_m}{R_L} \Rightarrow 50mA$$

$$I_{DC} = \frac{I_m}{\pi} \Rightarrow 15.92mA$$

$$V_{DC} = \frac{V_m}{\pi} \Rightarrow 15.92V$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \Rightarrow 25mA$$

$$V_{\text{rms}} = 25\text{V}$$
$$\text{Efficiency}(\eta) = \frac{P_{\text{DC}}}{P_{\text{ac}}}$$
$$P_{\text{DC}} = I_{\text{DC}}^2 * R_L \Rightarrow 253.44\text{mW}$$
$$P_{\text{ac}} = I_{\text{rms}}^2 * R_L \Rightarrow 625\text{mW}$$
$$\eta = \frac{P_{\text{DC}}}{P_{\text{ac}}} \Rightarrow 0.405 \text{ or } 40.05\%$$
$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{\text{rms}}}{I_{\text{DC}}}\right)^2 - 1}$$
$$\gamma = 1.21$$

P2. A diode with forward resistance of 25 Ohms in an Half wave rectifier circuit energized by a 50V peak sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor.

Given data:

To find: Solution:

H $V_m = 50\text{V}, R_L = 1\text{K}\Omega, R_f = 25\text{ Ohms}$

$$I_{\text{DC}}, V_{\text{DC}}, I_{\text{rms}}, V_{\text{rms}}, \eta \text{ and } \gamma$$
$$I_m = \frac{V_m}{R_f + R_L} \Rightarrow 48.78\text{mA}$$
$$I_{\text{DC}} = \frac{I_m}{\pi} \Rightarrow 15.53\text{mA}$$

W
R

$$\begin{aligned}
 V_{DC} &= I_{DC} * R_L \Rightarrow 15.53V \\
 I_{rms} &= \frac{I_m}{2} \Rightarrow 24.39mA \\
 V_{rms} &= I_{rms}(R_f + R_L) = 24.99V \\
 \text{Efficiency}(\eta) &= \frac{P_{DC}}{P_{ac}} \\
 P_{DC} &= I_{DC}^2 * R_L \Rightarrow 241.18mW \\
 P_{ac} &= I_{rms}^2 * (R_L + R_f) \Rightarrow 609.74mW \\
 \eta &= \frac{P_{DC}}{P_{ac}} \Rightarrow 0.3955 \text{ or } 39.55\% \\
 \text{Ripple factor}(\gamma) &= \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1} \\
 \gamma &= 1.211
 \end{aligned}$$

P3. A diode with forward resistance of 25 Ohms in an Half wave rectifier circuit energized by a 50V peak sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor. Assume the internal resistance of the secondary of the transformer is 25 Ohms.

Given data:

$$\text{HWR, } V_m = 50 \text{ V, } R_L = 1K\Omega, R_f = 25 \text{ Ohms, } R_s = 25$$

Ohms To find:

$$I_{DC}, V_{DC}, I_{rms}, V_{rms}, \eta \text{ and } \gamma$$

Solution:

$$\begin{aligned}
 I_m &= \frac{V_m}{R_f + R_s + R_L} \Rightarrow 47.61mA \\
 I_{DC} &= \frac{I_m}{\pi} \Rightarrow 15.16mA \\
 V_{DC} &= I_{DC} * R_L \Rightarrow 15.16V \\
 I_{rms} &= \frac{I_m}{2} \Rightarrow 23.58mA \\
 V_{rms} &= I_{rms}(R_f + R_s + R_L) = 24.76V \\
 \text{Efficiency}(\eta) &= \frac{P_{DC}}{P_{ac}} \\
 P_{DC} &= I_{DC}^2 * R_L \Rightarrow 229.82mW \\
 P_{ac} &= I_{rms}^2 * (R_L + R_f + R_s) \Rightarrow 583.81mW \\
 \eta &= \frac{P_{DC}}{P_{ac}} \Rightarrow 0.3936 \text{ or } 39.36\% \\
 \text{Ripple factor}(\gamma) &= \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1} \\
 \gamma &= 1.19
 \end{aligned}$$

P4. A diode with forward resistance of 25 Ohms in an Half wave rectifier circuit energized by a secondary voltage of 35.35V rms sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of

1 K ohms, also find efficiency and ripple factor. Assume the internal resistance of the secondary of the transformer is 25 Ohms.

Given data:

Solution: –

To find:

H DC, I_{rms} , V_{rms} , η and γ

W

R $V_m = \sqrt{2}V_s => 50V$

,
V

Er. Vinita kumara, YBN University, Ranchi

s
(
r
m
s
)
=
3
5
.
3
5
V
,
R
L
=
1
K
Ω
,
R
f
=
2
5
0
h
m
s
,
R
s
=
2
5
0
h
m
s

I
D
C
,
V

$$I_m = \frac{V_m}{R_f + R_s + R_L} \Rightarrow 47.61\text{mA}$$

$$I_{DC} = \frac{I_m}{\pi} \Rightarrow 15.16\text{mA}$$

$$V_{DC} = I_{DC} * R_L \Rightarrow 15.16\text{V}$$

$$I_{rms} = \frac{I_m}{2} \Rightarrow 23.58\text{mA}$$

$$V_{rms} = I_{rms}(R_f + R_s + R_L) = 24.76\text{V}$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 229.82\text{mW}$$

$$P_{ac} = I_{rms}^2 * (R_L + R_f + R_s) \Rightarrow 583.81\text{mW}$$

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.3936 \text{ or } 39.36\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1}$$

$$\gamma = 1.19$$

P5. A diode with forward resistance of 25 Ohms in an Half wave rectifier circuit is energized by a secondary voltage of 70.7V peak to peak rms sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor. Assume the internal resistance of the secondary of the transformer is 25 Ohms.

Given data:

$$\text{HWR, } V_{s(\text{rms})\text{P-P}} = 70.7 \text{ V, } R_L = 1\text{K}\Omega, R_f = 25 \text{ Ohms, } R_s = 25$$

Ohms To find:

$$I_{DC}, V_{DC}, I_{rms}, V_{rms}, \eta \text{ and } \gamma$$

Solution:

$$V_m = \frac{\sqrt{2}V_s}{2} \Rightarrow 50V$$

$$I_m = \frac{V_m}{R_f + R_s + R_L} \Rightarrow 47.61mA$$

$$I_{DC} = \frac{I_m}{\pi} \Rightarrow 15.16mA$$

$$V_{DC} = I_{DC} * R_L \Rightarrow 15.16V$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \Rightarrow 23.58mA$$

$$V_{rms} = I_{rms}(R_f + R_s + R_L) = 24.76V$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 229.82mW$$

$$P_{ac} = I_{rms}^2 * (R_L + R_f + R_s) \Rightarrow 583.81mW$$

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.3936 \text{ or } 39.36\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1}$$

$$\gamma = 1.19$$

P6. A diode with forward resistance of 25 Ohms in an Half wave rectifier circuit is energized by a transformer of turns ratio 5:1 and primary voltage of 176.75V sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor. Assume the internal resistance of the secondary of the transformer is 25 Ohms.

Given data:

HWR, $V_p(\text{rms}) = 176.75 \text{ V}$, $R_L = 1\text{K}\Omega$, $R_f = 25 \text{ Ohms}$, $R_s = 25$

Ohms **To find:**

I_{DC} , V_{DC} , I_{rms} , V_{rms} , η and γ

Solution:

$$V_{s(\text{rms})} = \frac{V_p}{5} \quad (\text{Since } \frac{N_1}{N_2} = \frac{V_p}{V_s})$$

$$V_{s(\text{rms})} = 35.35 \text{ Volts}$$

$$V_m = \sqrt{2}V_s \Rightarrow 50\text{V}$$

$$I_m = \frac{V_m}{R_f + R_s + R_L} \Rightarrow 47.61\text{mA}$$

$$I_{DC} = \frac{I_m}{\pi} \Rightarrow 15.16\text{mA}$$

$$V_{DC} = I_{DC} * R_L \Rightarrow 15.16\text{V}$$

$$I_{\text{rms}} = \frac{I_m}{2} \Rightarrow 23.58\text{mA}$$

$$V_{\text{rms}} = I_{\text{rms}}(R_f + R_s + R_L) = 24.76\text{V}$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 229.82\text{mW}$$

$$P_{ac} = I_{\text{rms}}^2 * (R_L + R_f + R_s) \Rightarrow 583.81\text{mW}$$

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.3936 \text{ or } 39.36\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{\text{rms}}}{I_{DC}}\right)^2 - 1}$$

$$\gamma = 1.19$$

P7. A diode with forward resistance of 25 Ohms in an Half wave rectifier circuit is energized by a $50\sin 314t$ supply. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor. Assume the internal resistance of the secondary of the transformer is 25 Ohms. Also find the frequency of the output signal and PIV.

Given data:

HWR, $v_i = 50\sin\omega t \text{ V}$, $R_L = 1\text{K}\Omega$, $R_f = 25 \text{ Ohms}$, $R_s = 25 \text{ Ohms}$, $\omega = 314 \frac{\text{rad}}{\text{sec}}$

To find:

Er. Vinita kumara, YBN University, Ranchi

$$V_{rms} = I_{rms}(R_f + R_s + R_L) = 24.76V$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 229.82mW$$

$$P_{ac} = I_{rms}^2 * (R_L + R_f + R_s) \Rightarrow 583.81mW$$

$I_{DC}, V_{DC}, I_{rms}, V_{rms}, \eta$ and γ

Solution:

$$v_i = v_m \sin \omega t \Rightarrow 50 \sin \omega t$$

$$V_m = 50V$$

$$I_m = \frac{V_m}{R_f + R_s + R_L} \Rightarrow 47.61mA$$

$$I_{DC} = \frac{I_m}{\pi} \Rightarrow 15.16mA$$

$$V_{DC} = I_{DC} * R_L \Rightarrow 15.16V$$

$$I_{rms} = \frac{I_m}{2} \Rightarrow 23.58mA$$

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.3936 \text{ or } 39.36\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1}$$

$$\gamma = 1.19$$

$$\omega = 2\pi f_{in}$$

$$f_{in} = 50\text{Hz}$$

$$f_{out} = f_{in} \Rightarrow 50\text{Hz.}$$

$$\text{PIV} = V_m \Rightarrow 50\text{V}$$

P8. An HWR generates 30W DC power from 120W of AC input power.

(i) What is the rectification efficiency?

(ii) What happens to remaining 90 watts?

Given data:

$$P_{DC} = 30 \text{ Watts} \quad P_{ac} = 120 \text{ Watts}$$

To find: η , reason for lost of remaining 90W **Solution:**

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 25\%$$

25% rectification efficiency does not implies that, the remaining 90W power is wasted in the circuit. Out of 120W, 60W for positive half cycle and remaining 60W for negative half cycle. Also the internal resistance of the circuit affects the delivered output. Actually, power efficiency is $\frac{30\text{w}}{60\text{w}} \Rightarrow 50\%$.

That is, half wave rectifier accepts only 60W input power and converts into 30W DC.

Therefore, it is appropriate to say that efficiency of rectification is 25% and not 50% which is power efficiency.

P9. Design an HWR circuit by using a transformer of turns ratio 10:1 to supply 5V DC voltage to 1K Ohms load resistor, the diode has 25 ohms internal forward resistance and 25 Ohms of transformer resistance. Given data:

$$N_1: N_2 = 10:1, V_{DC} = 5\text{V}, R_L = 1\text{K}\Omega, R_{diode} = 25\Omega, R_{tr} = 25\Omega$$

$$V_{ac} = V_p$$

To find:

Solution:

Er. Vinita kumara, YBN University, Raichur

$$V_{DC} = \sqrt{2} \left(\frac{V_P}{10} \right) \frac{1000}{25 + 25 + 1000}$$

$$V_P = 37.123V(\text{rms})$$

$$V_{DC} = I_{DC} * R_L$$

$$I_{DC} = \frac{I_m}{\pi}$$

$$V_{DC} = \frac{I_m}{\pi} * R_L$$

$$I_m = \frac{V_m}{R_f + R_s + R_L}$$

$$V_{DC} = V_m * \frac{R_L}{R_f + R_s + R_L}$$

$$V = \frac{V_P}{10} \quad (\text{Since, } \frac{N_1}{N_2} = \frac{V_P}{V_S})$$

$$V_{DC} = \sqrt{2} \left(\frac{V_P}{10} \right) \frac{R_L}{R_f + R_s + R_L}$$

P10. A half wave rectifier circuit is energized by an AC supply of frequency 50Hz. Find the ripple voltage and ripple factor, if the load of 1K ohms connected across a capacitor of 100uF. Peak value of the unfiltered rectified output is 15 Volts.

Given data:

$$R_L = 1K\Omega, C = 100\mu F, f = 50\text{Hz}, V_p$$

= 15V **To find:**

$$V_{r(p-p)}, \gamma$$

Solution:

$$V_{r(p-p)} = \frac{V}{fR_L C} \Rightarrow 3V$$
$$\text{Ripple factor}(\gamma) = \frac{1}{2\sqrt{3}fR_L C} \Rightarrow 0.0577$$

P11. An ideal diode in a 2 diodes /center tapped transformer Full wave rectifier circuit energized by a 50V peak sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor.

Given data:

$$\text{CTT} - \text{FWR}, V_m = 50 \text{ V}, R_L$$

= 1KΩ **To find:**

$$I_{DC}, V_{DC}, I_{rms}, V_{rms}, \eta \text{ and } \gamma$$

Solution:

$$I_m = \frac{V_m}{R_L} \Rightarrow 50\text{mA}$$

$$I_{DC} = \frac{2I_m R_L}{\pi} \Rightarrow 31.84\text{mA}$$

$$V_{DC} = \frac{2V_m}{\pi} \Rightarrow 31.84\text{V}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \Rightarrow 35.35\text{mA}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{rms} = 35.35\text{V}$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 1.0137\text{W}$$

$$P_{ac} = I_{rms}^2 * R_L \Rightarrow 1.249\text{W}$$

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.811 \text{ or } 81.1\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1}$$

$$\gamma = 0.4823$$

P12. A diode with forward resistance of 25 Ohms in a center tapped transformer full wave rectifier circuit energized by a 50V peak sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor.

Given data:

FWR, $V_m = 50\text{ V}$, $R_L = 1\text{K}\Omega$, $R_f = 25\text{ Ohms}$

To find:

I_{DC} , V_{DC} , I_{rms} , V_{rms} , η and γ

Solution:

$$I_m = \frac{V_m}{R_f + R_L} \Rightarrow 48.78\text{mA}$$

$$I_{DC} = \frac{2I_m}{\pi} \Rightarrow 31.07\text{mA}$$

$$V_{DC} = I_{DC} * R_L \Rightarrow 31.07\text{V}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \Rightarrow 34.49\text{mA}$$

$$V_{rms} = I_{rms}(R_f + R_L) \Rightarrow 35.35\text{V}$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 965.34\text{mW}$$

$$P_{ac} = I_{rms}^2 * (R_L + R_f) \Rightarrow 1.219\text{W}$$

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.7919 \text{ or } 79.19\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1}$$

$$\gamma = 0.4819$$

P13. A diode with forward resistance of 25 Ohms in a center tapped transformer full wave rectifier circuit energized by a 50V peak sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor. Assume the internal resistance of the secondary of the transformer is 25 Ohms.

Given data:

FWR, $V_m = 50\text{ V}$, $R_L = 1\text{K}\Omega$, $R_f = 25\text{ Ohms}$, $R_s = 25$

To find:

I_{DC} , V_{DC} , I_{rms} , V_{rms} , η and γ

Solution:

$$I_m = \frac{V_m}{R_f + R_s + R_L} \Rightarrow 47.61\text{mA}$$

$$I_{DC} = \frac{2I_m}{\pi} \Rightarrow 30.32\text{mA}$$

$$V_{DC} = I_{DC} * R_L \Rightarrow 30.32\text{V}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \Rightarrow 33.66\text{mA}$$

$$V_{rms} = I_{rms}(R_f + R_s + R_L) = 35.34\text{V}$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 919.3\text{mW}$$

$$P_{ac} = I_{rms}^2 * (R_L + R_f + R_s) \Rightarrow 1.189\text{W}$$

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.773 \text{ or } 77.3\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{rms}^2}{I_{DC}^2} - 1 \right)} \quad \gamma = 0.482$$

P14. A diode with forward resistance of 25 Ohms in a center tapped transformer full wave rectifier circuit energized by a secondary voltage of each half of the

transformer is 35.35V rms sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor. Assume the internal resistance of the secondary of the transformer is 25 Ohms.

Given data:

FWR, $V_{s(rms)} = 35.35\text{ V}$, $R_L = 1\text{K}\Omega$, $R_f = 25\text{ Ohms}$, $R_s = 25\text{ Ohms}$ **To find:**

I_{DC} , V_{DC} , I_{rms} , V_{rms} , η and γ

$$V_m = \sqrt{2}V_s \Rightarrow 50\text{V}$$

Solution:

$$I_m = \frac{V_m}{R_f + R_s + R_L} \Rightarrow 47.61\text{mA}$$

$$I_{DC} = \frac{2I_m}{\pi} \Rightarrow 30.32\text{mA}$$

$$V_{DC} = I_{DC} * R_L \Rightarrow 30.32\text{V}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \Rightarrow 33.66\text{mA}$$

$$V_{rms} = I_{rms}(R_f + R_s + R_L) = 35.34\text{V}$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 919.3\text{mW}$$

$$P_{ac} = I_{rms}^2 * (R_L + R_f + R_s) \Rightarrow 1.189\text{W}$$

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.773 \text{ or } 77.3\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1}$$

$$\gamma = 0.482$$

P15. A diode with forward resistance of 25 Ohms in a center tapped transformer full wave rectifier circuit is energized by a secondary voltage of each half of the transformer is 70.7V peak to peak rms sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor. Assume the internal resistance of the secondary of the transformer is 25 Ohms.

Given data:

FWR, $V_{s(rms)P-P} = 70.7\text{ V}$, $R_L = 1\text{K}\Omega$, $R_f = 25\text{ Ohms}$, $R_s = 25\text{ Ohms}$

To find:

I_{DC} , V_{DC} , I_{rms} , V_{rms} , η and γ

Solution:

$$V_m = \frac{\sqrt{2}V_s}{2} \Rightarrow 50\text{V}$$

$$I_m = \frac{V_m}{R_f + R_s + R_L} \Rightarrow 47.61\text{mA}$$

$$I_{DC} = \frac{2I_m}{\pi} \Rightarrow 30.32\text{mA}$$

$$V_{DC} = I_{DC} * R_L \Rightarrow 30.32\text{V}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \Rightarrow 33.66\text{mA}$$

$\sqrt{2}$

$$V_{rms} = I_{rms}(R_f + R_s + R_L) = 35.34\text{V}$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 919.3\text{mW}$$

$$P_{ac} = I_{rms}^2 * (R_L + R_f + R_s) \Rightarrow 1.189\text{W}$$

—

—

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.773 \text{ or } 77.3\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1}$$

$$\gamma = 0.482$$

P16. A diode with forward resistance of 25 Ohms in a center tapped transformer full wave rectifier circuit is energized by a transformer of turns ratio 5:1 and primary voltage of 353.5V sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor. Assume the internal resistance of the secondary of the transformer is 25 Ohms.

Given data:

$$\text{HWR, } V_P(\text{rms}) = 176.75 \text{ V, } R_L = 1\text{K}\Omega, R_f = 25 \text{ Ohms, } R_s = 25$$

Ohms To find:

$$I_{DC}, V_{DC}, I_{rms}, V_{rms}, \eta \text{ and } \gamma$$

Solution:

$$V_{s(\text{rms})} = \frac{V_P}{5} \quad \left(\text{Since } \frac{N_1}{N_2} = \frac{V_P}{V_s}\right)$$

$$V_{s(\text{rms})} = 70.7 \text{ Volts (total secondary voltage)}$$

$$V_{s(\text{rms})} = 35.35 \text{ Volts (for each half of the transformer)}$$

$$V_m = \sqrt{2}V_s \Rightarrow 50\text{V}$$

$$I_m = \frac{V_m}{R_f + R_s + R_L} \Rightarrow 47.61\text{mA}$$

$$I_{DC} = \frac{2I_m}{\pi} \Rightarrow 30.32\text{mA}$$

$$V_{DC} = I_{DC} * R_L \Rightarrow 30.32\text{V}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \Rightarrow 33.66\text{mA}$$

$$V_{rms} = I_{rms}(R_f + R_s + R_L) = 35.34\text{V}$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 919.3\text{mW}$$

$$P_{ac} = I_{rms}^2 * (R_L + R_f + R_s) \Rightarrow 1.189\text{W}$$

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.773 \text{ or } 77.3\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1}$$

$$\gamma = 0.482$$

P17. A diode with forward resistance of 25 Ohms in a center tapped transformer full wave rectifier circuit is energized by a $50\sin 314t$ supply. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor. Assume the internal resistance of the secondary of the transformer is 25 Ohms. Also find the frequency of the output signal and PIV.

Given data:

$$v_i = 50\sin\omega t \quad R_f = 25 \text{ Ohms}, R_s = 25 \text{ Ohms}, R_L = 1 \text{ K}\Omega, \omega = 314 \frac{\text{rad}}{\text{sec.}}$$

To find:

$$I_{DC}, V_{DC}, I_{rms}, V_{rms}, \eta \text{ and } \gamma$$

Solution:

$$v_i = v_m \sin\omega t \Rightarrow 50\sin\omega t$$

$$V_m = 50V$$

$$I_m = \frac{V_m}{R_f + R_s + R_L} \Rightarrow 47.61mA$$

$$I_{DC} = \frac{2I_m}{\pi} \Rightarrow 30.32mA$$

$$V_{DC} = I_{DC} * R_L \Rightarrow 30.32V$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \Rightarrow 33.66mA$$

$$V_{rms} = I_{rms}(R_f + R_s + R_L) = 35.34V$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 919.3mW$$

$$P_{ac} = I_{rms}^2 * (R_L + R_f + R_s) \Rightarrow 1.189W$$

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.773 \text{ or } 77.3\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1}$$

$$\gamma = 0.482$$

$$f_{in} = \frac{\omega}{2\pi} \Rightarrow 50Hz.$$

$$f_{out} = 2f_{in} \Rightarrow 100Hz.$$

$$PIV = 2V_m \Rightarrow 100V$$

P18. A FWR generates 90W DC power from 120W of AC input power.

(i) What is the rectification efficiency?

(ii) What happens to remaining 30 watts?

Given data:

$$P_{DC} = 90 \text{ Watts}$$

$$P_{ac} = 120 \text{ Watts}$$

To find: η , reason for lost of remaining 90W **Solution:**

i)
$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 75\%$$

ii) Rectification efficiency is 75% and the remaining 25% power wasted due to internal resistances of the diode as well as transformer.

P19. Design an FWR circuit by using a transformer of turns ratio 10:1 to supply 5V DC voltage to 1K Ohms load resistor, the diode has 25 ohms internal forward resistance and 25 Ohms of transformer resistance.

Given data:

$$N_1 : N_2 = 10 : 1, V_{DC} = 5V, R_f = R_s = 25\Omega, R_L = 1K\Omega$$

To find:

$$V_{ac} = V_P$$

Solution:

Er. Vinita kumara, YBN University, Ranchi $I_m = \frac{2V_m}{R_f + R_s + R_L}$

$$V_{DC} = 2V_m * \frac{R_L}{R_f + R_s + R_L}$$

$$V_{DC} = I_{DC} * R_L$$

$$I_{DC} = \frac{2I_m}{\pi}$$

$$V_{DC} = \frac{2I_m}{\pi} * R_L$$

$$V_m = \frac{\sqrt{2}V_s}{N_1} = \frac{V_p}{N_2}$$

$$V = \frac{V_p}{10} \quad (\text{Since, } \frac{N_1}{N_2} = \frac{V_p}{V_s})$$

$$V_{DC} = \frac{2\sqrt{2}}{2} \left(\frac{V_p}{10} \right) \frac{R_L}{R_f + R_s + R_L}$$

$$5 = \sqrt{2} \left(\frac{V_p}{10} \right) \frac{1000}{25 + 25 + 1000}$$

$$V_p = 148.48V(\text{rms})$$

P20. A center tapped transformer full wave rectifier circuit is energized by an AC supply of frequency 50Hz. Find the ripple voltage and ripple factor, if the load of 1K ohms connected across a capacitor of 100uF. Peak value of the unfiltered rectified output is 15 Volts.

Given data:

$$R_L = 1K\Omega, C = 100\mu F, f = 50\text{Hz}, V_p = 15V$$

To find:

$$V_{r(p-p)}, \gamma$$

Solution:

$$V_{r(p-p)} = \frac{V}{2fR_L C} \Rightarrow 1.5V$$

$$\text{Ripple factor}(\gamma) = \frac{1}{4\sqrt{3}fR_L C} \Rightarrow 0.0288$$

P21. A bridge type full wave rectifier circuit energized by a 50V peak sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor.

Given data:

$$\text{BT - FWR, } V_m = 50V, R_L$$

= 1KΩ To find:

$$I_{DC}, V_{DC}, I_{rms}, V_{rms}, \eta \text{ and } \gamma$$

Solution:

Er. Vinita kumara, YBN University, Ranchi

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 1.0137W$$

$$P_{ac} = I_{rms}^2 * R_L \Rightarrow 1.249W$$

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.811 \text{ or } 81.1\%$$

$$I_m = \frac{V_m}{R_L} \Rightarrow 50mA$$

$$I_{DC} = \frac{2I_m}{\pi} \Rightarrow 31.84mA$$

$$V_{DC} = \frac{2V_m}{\pi} \Rightarrow 31.84V$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \Rightarrow 35.35mA$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{rms} = 35.35V$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{\text{rms}}}{I_{\text{DC}}}\right)^2 - 1}$$

$$\gamma = 0.4823$$

P22. A diode with forward resistance of 25 Ohms in a bridge type full wave rectifier circuit energized by a 50V peak sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor.

Given data:

$$\text{FWR, } V_m = 50 \text{ V, } R_L = 1\text{K}\Omega, R_f = 25$$

Ohms To find:

$$I_{\text{DC}}, V_{\text{DC}}, I_{\text{rms}}, V_{\text{rms}}, \eta \text{ and } \gamma$$

Solution:

$$I_m = \frac{V_m}{2R_f + R_L} \Rightarrow 47.61\text{mA}$$

$$I_{\text{DC}} = \frac{I_m}{\pi} \Rightarrow 30.32\text{mA}$$

$$V_{\text{DC}} = I_{\text{DC}} * R_L \Rightarrow 30.32\text{V}$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}} \Rightarrow 33.66\text{mA}$$

$$V_{\text{rms}} = I_{\text{rms}}(2R_f + R_L) = 35.34\text{V}$$

$$\text{Efficiency}(\eta) = \frac{P_{\text{DC}}}{P_{\text{ac}}}$$

$$P_{\text{DC}} = I_{\text{DC}}^2 * R_L \Rightarrow 919.3\text{mW}$$

$$P_{\text{ac}} = I_{\text{rms}}^2 * (R_L + 2R_f) \Rightarrow 1.189\text{W}$$

$$\eta = \frac{P_{\text{DC}}}{P_{\text{ac}}} \Rightarrow 0.773 \text{ or } 77.3\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{\text{rms}}}{I_{\text{DC}}}\right)^2 - 1}$$

$$\gamma = 0.482$$

P23. A diode with forward resistance of 25 Ohms in a bridge type full wave rectifier circuit energized by a 50V peak sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor. Assume the internal resistance of the secondary of the transformer is 25 Ohms.

Given data:

$$\text{FWR, } V_m = 50 \text{ V, } R_L = 1\text{K}\Omega, R_f = 25 \text{ Ohms, } R_s = 25$$

Ohms To find:

$$I_{\text{DC}}, V_{\text{DC}}, I_{\text{rms}}, V_{\text{rms}}, \eta \text{ and } \gamma$$

Solution:

Er. Vinita kumara, YBN University, Ranchi

$$V_{DC} = I_{DC} * R_L \Rightarrow 29.62V$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \Rightarrow 32.88mA$$

$$V_{rms} = I_{rms}(2R_f + R_s + R_L) = 35.34V$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$I_m = \frac{V_m}{2R_f + R_s + R_L} \Rightarrow 46.51mA$$

$$I_{DC} = \frac{2I_m}{\pi} \Rightarrow 29.62mA$$

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 877.34mW$$

$$P_{ac} = I_{rms}^2 * (R_L + 2R_f + R_s) \Rightarrow 1.162W$$

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.755 \text{ or } 75.5\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1}$$

$$\gamma = 0.4819$$

P24. A diode with forward resistance of 25 Ohms in a bridge type full wave rectifier circuit energized by a secondary voltage of 35.35V rms sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor. Assume the internal resistance of the secondary of the transformer is 25 Ohms.

Given data:

FWR, $V_{s(rms)} = 35.35 \text{ V}$, $R_L = 1K\Omega$, $R_f = 25 \text{ Ohms}$, $R_s = 25 \text{ Ohms}$ **To find:**

DC, DC, rms, rms, η γ I V I V and

$$V_m = \sqrt{2}V_s \Rightarrow 50V$$

Solution:

$$I_m = \frac{V_m}{2R_f + R_s + R_L} \Rightarrow 46.51mA$$

$$I_{DC} = \frac{2I_m}{\pi} \Rightarrow 29.62mA$$

$$V_{DC} = I_{DC} * R_L \Rightarrow 29.62V$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \Rightarrow 32.88mA$$

$$V_{rms} = I_{rms}(2R_f + R_s + R_L) = 35.34V$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 877.34mW$$

$$P_{ac} = I_{rms}^2 * (R_L + 2R_f + R_s) \Rightarrow 1.162W$$

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.755 \text{ or } 75.5\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1}$$

$$\gamma = 0.4819$$

P25. A diode with forward resistance of 25 Ohms in a bridge type full wave rectifier circuit is energized by a secondary voltage of 70.7V peak to peak rms sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor.

Assume the internal resistance of the secondary of the transformer is 25 Ohms.

Given data:

—
HWR, $V_{s(rms)P-P} = 70.7 \text{ V}$, $R_L = 1\text{K}\Omega$, $R_f = 25 \text{ Ohms}$, $R_s = 25$

To find:

I_{DC} , V_{DC} , I_{rms} , V_{rms} , η and γ

Solution:

$$V_m = \frac{\sqrt{2}V_s}{2} \Rightarrow 50\text{V}$$

$$I_m = \frac{V_m}{2R_f + R_s + R_L} \Rightarrow 46.51\text{mA}$$

$$I_{DC} = \frac{2I_m}{\pi} \Rightarrow 29.62\text{mA}$$

$$V_{DC} = I_{DC} * R_L \Rightarrow 29.62\text{V}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \Rightarrow 32.88\text{mA}$$

$$V_{rms} = I_{rms}(2R_f + R_s + R_L) = 35.34\text{V}$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 877.34\text{mW}$$

$$P_{ac} = I_{rms}^2 * (R_L + 2R_f + R_s) \Rightarrow 1.162\text{W}$$

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.755 \text{ or } 75.5\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1}$$

$$\gamma = 0.4819$$

P26. A diode with forward resistance of 25 Ohms in a bridge type full wave rectifier circuit is energized by a transformer of turns ration 5:1 and primary voltage of 176.75V sinusoidal signal. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor. Assume the internal resistance of the secondary of the transformer is 25 Ohms.

Given data:

$$\text{HWR, } V_p(\text{rms}) = 176.75 \text{ V, } R_L = 1\text{K}\Omega, R_f = 25 \text{ Ohms, } R_s = 25$$

Ohms To find:

$$I_{DC}, V_{DC}, I_{rms}, V_{rms}, \eta \text{ and } \gamma$$

Solution:

$$V_{s(\text{rms})} = \frac{V_p}{5} \left(\text{Since } \frac{N_1}{N_2} = \frac{V_p}{V_s} \right)$$

$$\begin{aligned}
 V_{s(\text{rms})} &= 35.35 \text{ Volts} \\
 V_m &= \sqrt{2}V_s \Rightarrow 50\text{V} \\
 I_m &= \frac{V_m}{2R_f + R_s + R_L} \Rightarrow 46.51\text{mA} \\
 I_{\text{DC}} &= \frac{2I_m}{\pi} \Rightarrow 29.62\text{mA} \\
 V_{\text{DC}} &= I_{\text{DC}} * R_L \Rightarrow 29.62\text{V} \\
 I_{\text{rms}} &= \frac{I_m}{\sqrt{2}} \Rightarrow 32.88\text{mA} \\
 V_{\text{rms}} &= I_{\text{rms}}(2R_f + R_s + R_L) = 35.34\text{V} \\
 \text{Efficiency}(\eta) &= \frac{P_{\text{DC}}}{P_{\text{ac}}} \\
 P_{\text{DC}} &= I_{\text{DC}}^2 * R_L \Rightarrow 877.34\text{mW} \\
 P_{\text{ac}} &= I_{\text{rms}}^2 * (R_L + 2R_f + R_s) \Rightarrow 1.162\text{W} \\
 \eta &= \frac{P_{\text{DC}}}{P_{\text{ac}}} \Rightarrow 0.755 \text{ or } 75.5\%
 \end{aligned}$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{\text{rms}}}{I_{\text{DC}}} \right)^2 - 1} \quad \gamma = 0.4819$$

P27. A diode with forward resistance of 25 Ohms in a bridge type full wave rectifier circuit is energized by a $50\sin 314t$ supply. Find the DC current and voltage, rms current and voltage across a load of 1 K ohms, also find efficiency and ripple factor.

Assume the internal resistance of the secondary of the transformer is 25 Ohms. Also find the frequency of the output signal and PIV.

Given data:

$$\text{rad} \\ \text{HWR, } v_i = 50\sin\omega t \text{ V, } R_L = 1\text{K}\Omega, R_f = 25 \text{ Ohms, } R_s = 25 \text{ Ohms, } \omega = 314 \frac{\text{rad}}{\text{sec}}$$

To find:

$$I_{DC}, V_{DC}, I_{rms}, V_{rms}, \eta \text{ and } \gamma$$

Solution:

$$v_i = v_m \sin\omega t \Rightarrow 50\sin\omega t$$

$$V_m = 50\text{V}$$

$$I_m = \frac{V_m}{2R_f + R_s + R_L} \Rightarrow 46.51\text{mA}$$

$$I_{DC} = \frac{2I_m}{\pi} \Rightarrow 29.62\text{mA}$$

$$V_{DC} = I_{DC} * R_L \Rightarrow 29.62\text{V}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \Rightarrow 32.88\text{mA}$$

$$V_{rms} = I_{rms}(2R_f + R_s + R_L) = 35.34\text{V}$$

$$\text{Efficiency}(\eta) = \frac{P_{DC}}{P_{ac}}$$

$$P_{DC} = I_{DC}^2 * R_L \Rightarrow 877.34\text{mW}$$

$$P_{ac} = I_{rms}^2 * (R_L + 2R_f + R_s) \Rightarrow 1.162\text{W}$$

$$\eta = \frac{P_{DC}}{P_{ac}} \Rightarrow 0.755 \text{ or } 75.5\%$$

$$\text{Ripple factor}(\gamma) = \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1}$$

$$\gamma = 0.4819$$

$$f_{in} = \frac{\omega}{2\pi} \Rightarrow 50\text{Hz.}$$

$$f_{out} = 2f_{in} \Rightarrow 100\text{Hz.}$$

$$\text{PIV} = V_m \Rightarrow 50 \text{ V}$$

P28. The four diodes used in a bridge rectifier circuit have forward resistances which may be considered constant at 1Ω and infinite reverse resistance. The alternating supply voltage is 240 V r.m.s. and load resistance is 480 Ω. Calculate (i) mean load current and (ii) power dissipated in each diode.

Given data:

$$R_f = 1 \text{ Ohm, } V_s = 240\text{V (rms), } R_L = 480 \text{ Ohms, BT - FWR}$$

To find:

$$I_{DC}, P_{diss}(\text{across each diode})$$

Solution:

$$V_m = \sqrt{2} V_s \Rightarrow 339.41V$$

$$I_m = \frac{V_m}{R} \Rightarrow 0.704A$$

$$I_{DC} = \frac{2I_m}{\pi} \Rightarrow 0.448A$$

Er. Vinita kumara, YBN University, Ranchi

$$I_{rms}^2 \text{ (single diode)} = \frac{I_m^2}{2} \text{ (since, each diode conducts only half cycle)}$$

$$I_{rms} = 0.352A$$

$$P_{diss} \text{ (across each diode)} = 0.123W$$
